


What is LDO (Low-Dropout Voltage Regulator)



2006/6 John Wu
吳旻翰

- *What is LDO?*
- *Why use LDO?*
- *Major types of LDO*
- *How to select a LDO?*
- *Other design issue*

What is a LDO?

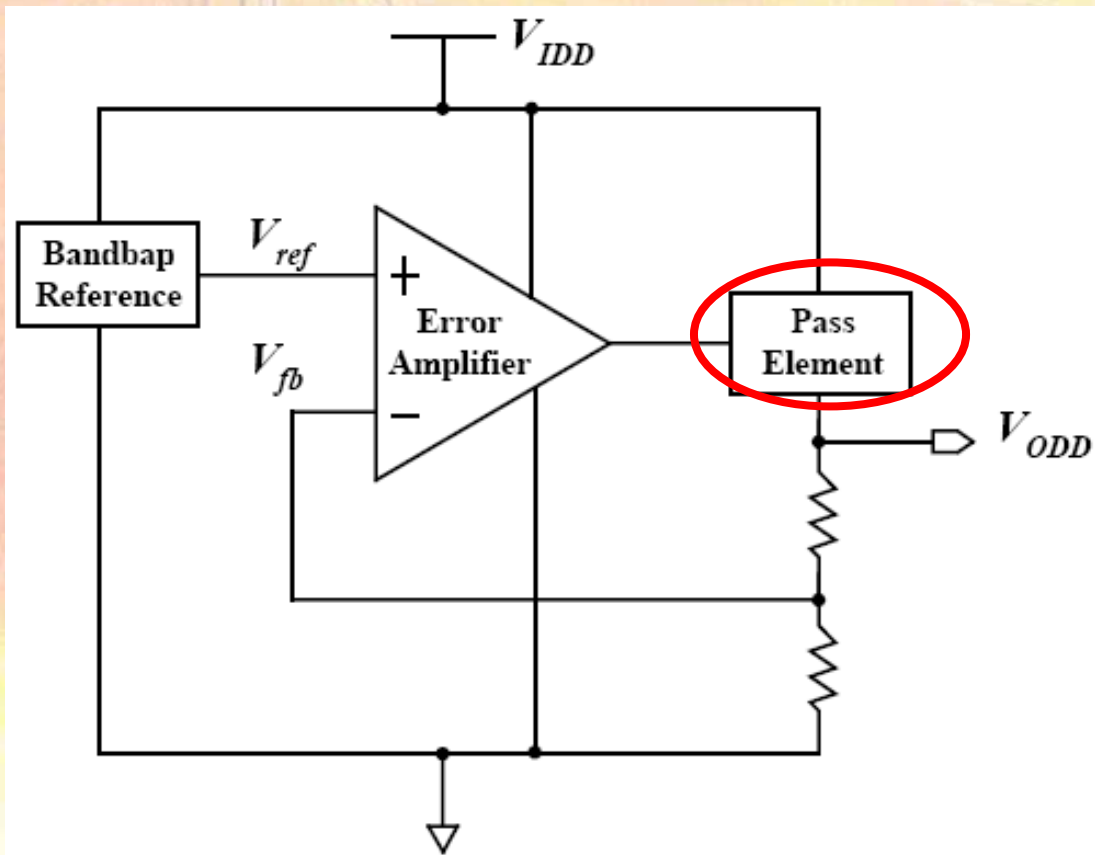


V_{IDD}: Input voltage
V_{ODD}: Output voltage

Basic LDO architecture


Techmosa *Pass elements of LDO*

Transistor:

PNP

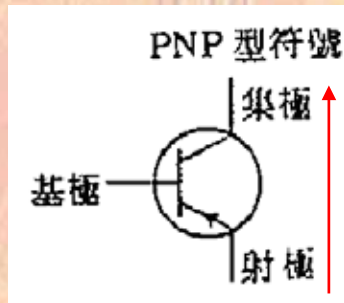


NPN

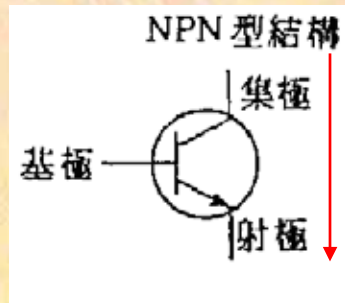


MOSFET:

N-MOS

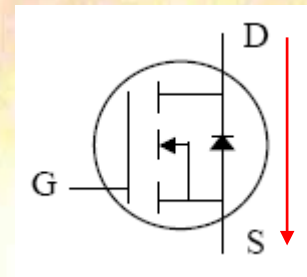

P-MOS

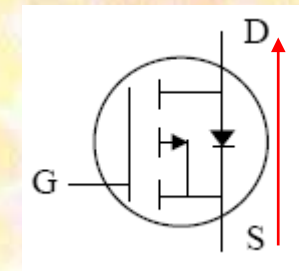

Transistor:

$$I_c = \beta * I_b$$

$$I_c = \beta * I_e$$

$$\beta = \beta / (\beta + 1) < 1$$


MOSFET:

Working on resistive region

$$I_D = K[2(V_{GS} - V_T) V_{DS} - V_{DS}^2]$$


V_T = threshold voltage

K = conductance parameter

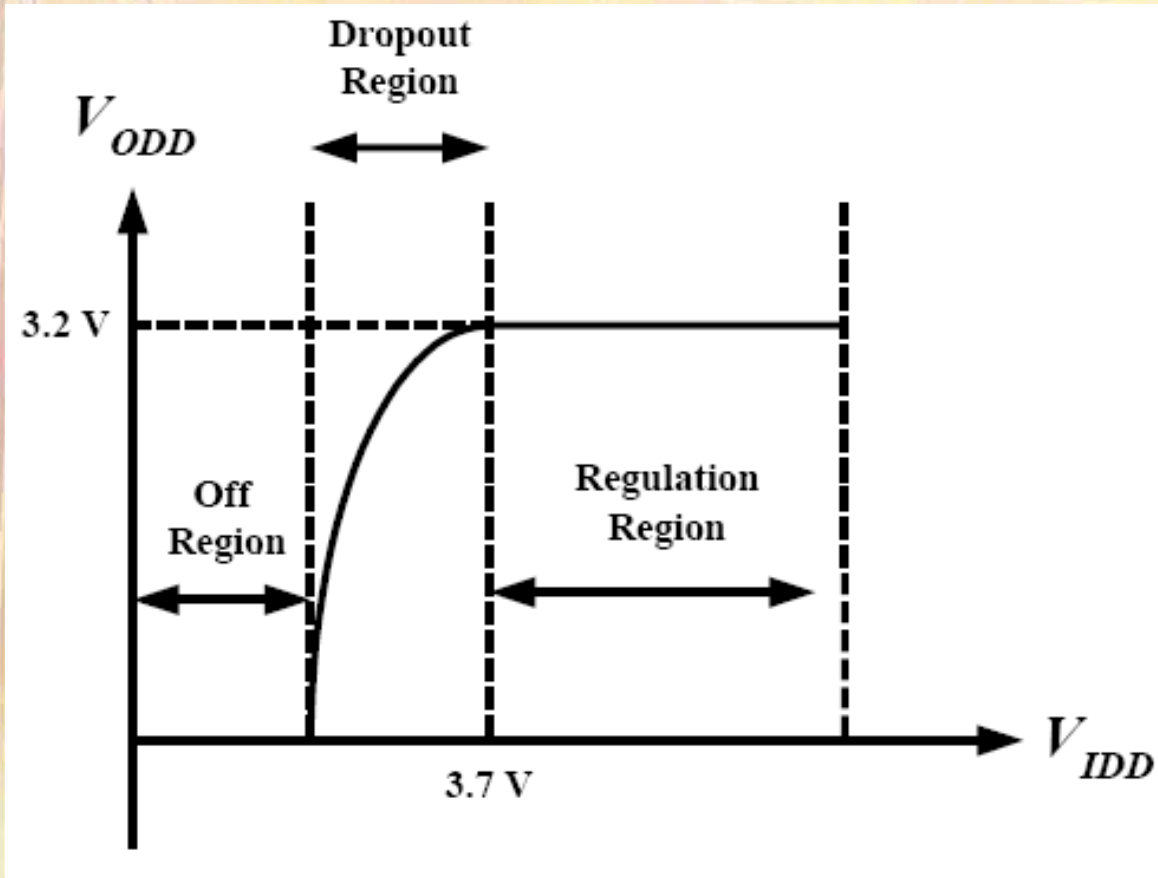

LDO input and output voltage

Why Linear?

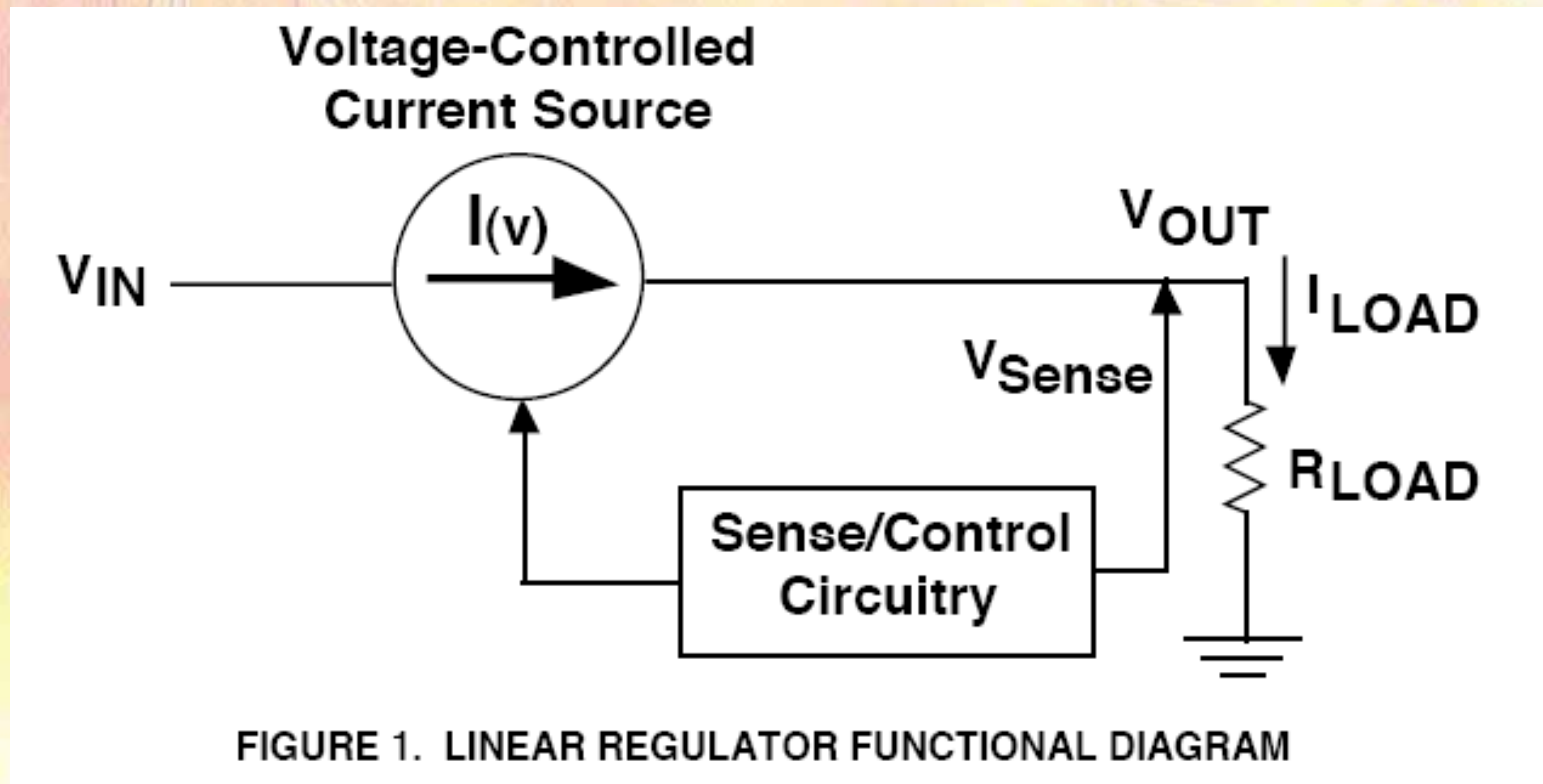


Why use LDO?

Benefits :

- ✓ Low cost & Easy-to-use
- ✓ Accurate supply voltage
- ✓ Active noise filtering
- ✓ Protection from over-current faults
- ✓ Generation of multiple output voltages from a Single source

Fault:

- ✓ Efficiency is bed
- ✓ Thermal issue

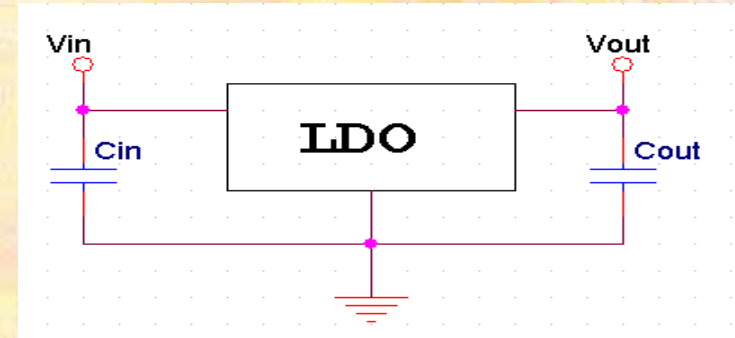


Why use LDO?

Who Prefers LDO?

- ✓ Communications equipment
- ✓ Small devices
- ✓ Battery operated systems
- ✓ Low current devices
- ✓ High performance microprocessors with sleep mode (fast transient recovery required)
- ✓ Analog Device (Audio power, RF power...)




Techmosa Major types of LDO

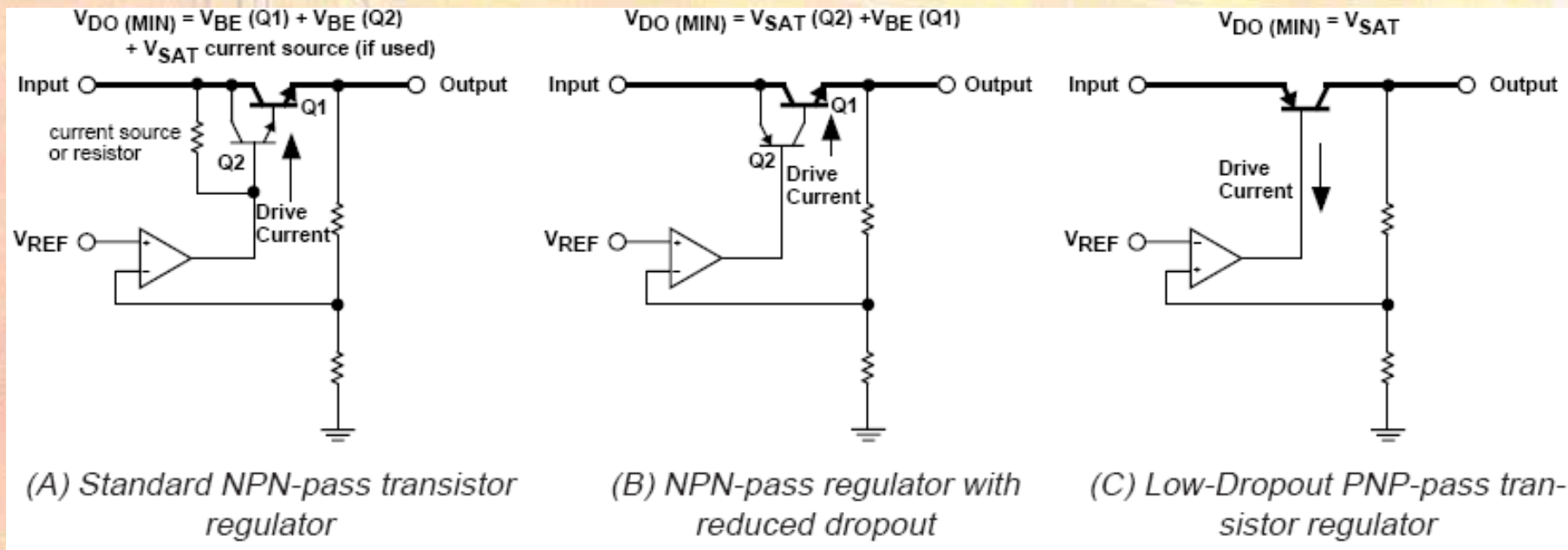


- (A) “Classic” NPN-based regulators that require 2.5 to 3V of excess input voltage to function. 7805, 317, 340
- (B) “Low Dropout NPN” regulators, with a NPN output but a PNP base drive circuit. These devices reduce the dropout requirement to 1.2 to 1.5V.
- (C) True low dropout PNP-based regulators that need 0.3V to 0.6V extra for operation.

Major types of LDO

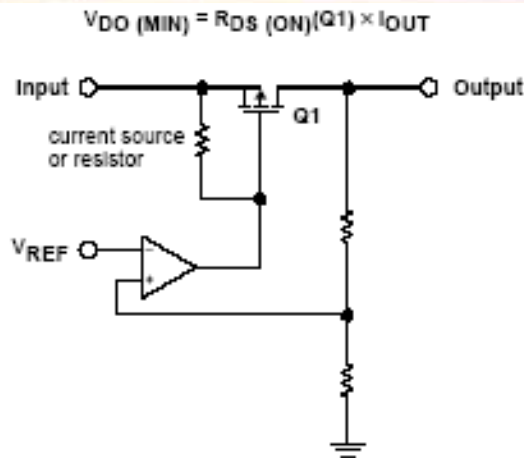

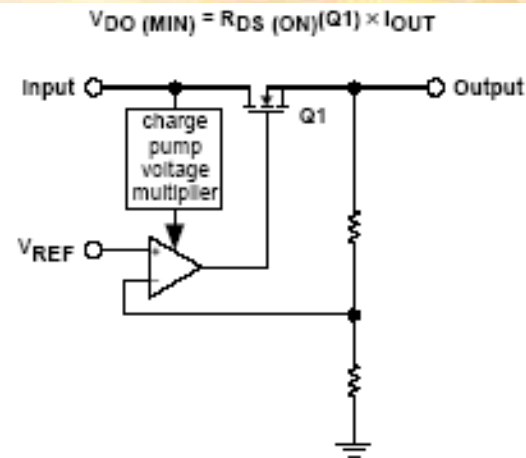(D) P-Channel MOSFET-pass transistor regulator



(E) N-Channel MOSFET-pass transistor regulator

(D) P-channel CMOS output regulators.

These devices have very low dropout voltages at low currents but require large die area (hence higher costly than bipolar versions)

(E) Regulator controllers.

Provide the control functions of a linear regulator, and do not have the pass element on it.

It provide the advantage of optimizing die area and cost for higher current applications.

Techmosa *Major types of LDO*

效能	Darlington	NPN	PNP	NMOS	PMOS
靜態電流	中等	中等	大	小	小
Dropout 電壓	$V_{EC(sat)}+2V_{BE}$	$V_{EC(sat)}+V_{BE}$	$V_{EC(sat)}$	$V_{SD(sat)}+V_{GS}$	$V_{SD(sat)}$
負載推動力	大	大	大	中等	中等
暫態反應速度	快	快	慢	中等	中等



各種傳輸元件的效能比較

%各有優劣%

Techmosa *How to select LDO?*

The most important parameters of LDO:

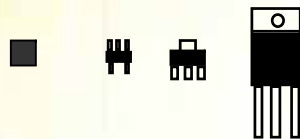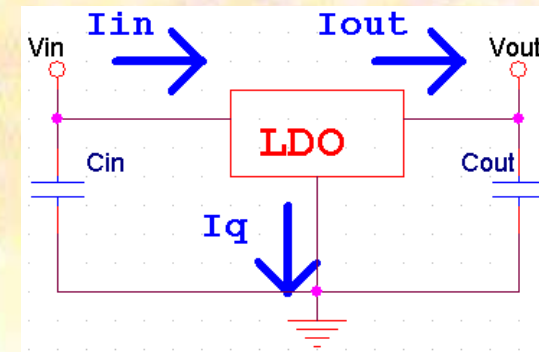- Input voltage (V_{in})
- Output voltage (V_{out})
- Maximum output current (I_{out})
- Dropout voltage
- Ground current /quiescent current (I_q)
- Power dissipation = $(V_{in}-V_{out}) * I_{out} + V_{in} * I_q$
- Package



Techmosa *Other design issue*


Component selection:

❑ *Input capacitor*

- Depends your V_{in} power quality.
- Larger values may be required if V_{in} has high ripple.
- X7R,X5R ceramic capacitor can be used for bypassing.

❑ *Output capacitor*

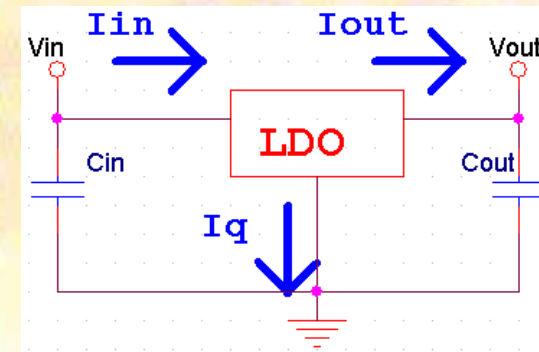- There is recommend minimum value of it.
- Compensation
- Low inductance, low ESR would be better.
- PNP&PMOS LDO need specified range ESR value.
- Exp: X7R,X5R,Tantalum



Techmosa *Other design issue*

❑ *LDO Efficiency:*



$$\text{Eff} = P_{\text{out}} / P_{\text{in}} = V_{\text{out}} \cdot I_{\text{out}} / V_{\text{in}} \cdot I_{\text{in}}$$

And, $I_{\text{out}} \approx I_{\text{in}}$

A close efficiency approximation: $\text{Eff} = V_{\text{out}} / V_{\text{in}}$

❑ *Power Supply Rejection Ratio(PSRR):*
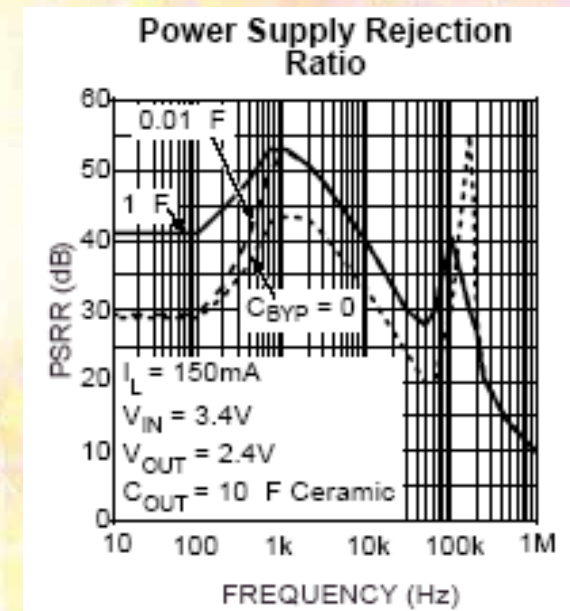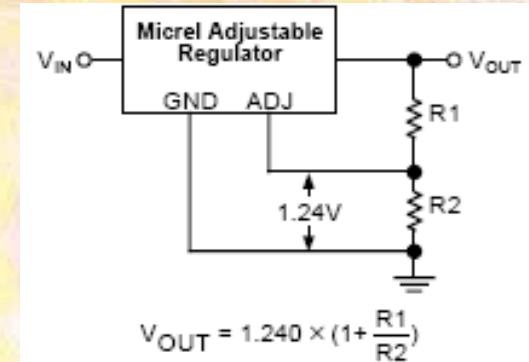
$$\text{PSRR}(\text{dB}) = 20 \log \left(\frac{V_{\text{in}}}{V_{\text{out}}} \right)$$



Techmosa *Other design issue*

❑ *Thermal Management*

- LDO power dissipation and heat-sink requirements for various 3.3V current levels.

Regulator	I _{OUT}	P _D (W)	θ _{SA} (°C/W)
MIC29150	1.25A	2.6	25
MIC29150	1.5A	3.2	21
MIC29300	2.0A	4.2	15
MIC29300	2.5A	5.2	11

- Θ Thermal resistance(C/W)
 $\Theta = T/Q$
 T: Temperature difference
 Q : Power dissipation
- Θ_{SA} : Heat Sink to Ambient (free air) Thermal resistance

- Ambient Temperature Affects Heat Sink Requirements

Output	Ambient Temperature		
	40°C	50°C	60°C
1.5A	24°C/W	21°C/W	17°C/W
5A	5.1°C/W	4.1°C/W	3.2°C/W

Techmosa *Other design issue*

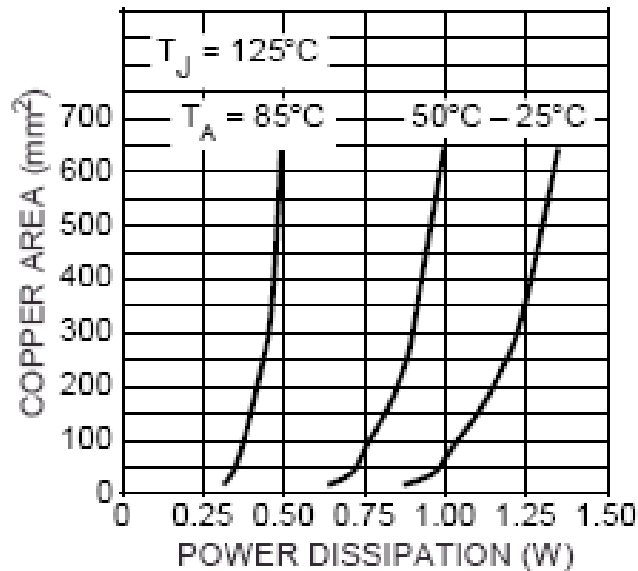



Figure 5. Copper Area vs. Power-SOIC Power Dissipation

The minimum amount of copper can be determined by knowing the maximum power dissipation required.

Techmosa *Other design issue*

What is a high performance LDO?

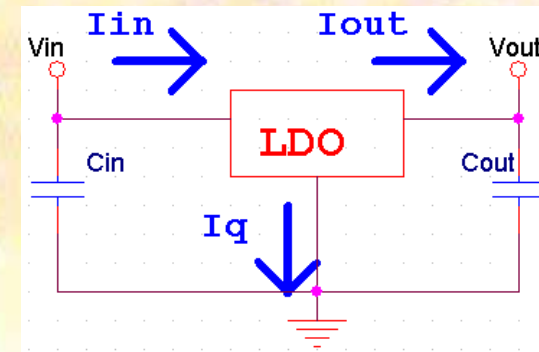- ✓ Wide V_{in} voltage range
- ✓ Low I_q current
- ✓ Low dropout voltage
- ✓ Small output capacitor
- ✓ High PSRR
- ✓ Over current protection
- ✓ Fast Transient Response
- ✓ Low Thermal resistance
- ✓ Small package





Thank You !